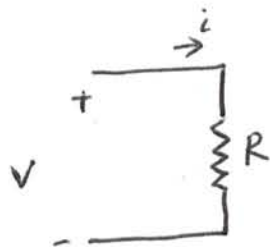


- i : Electric current (flow of electric charge)
- V : Voltage (electrical potential difference)
 $\Downarrow$
 (needs a reference)

Electrical Components:

1 - Resistor:




$$V = iR \rightarrow \text{Ohm } (\Omega)$$

$\swarrow \quad \searrow$
 Volts (V) Amp (A)

R = Resistance, $G = \frac{1}{R}$ = Conductance


2 - Capacitor:

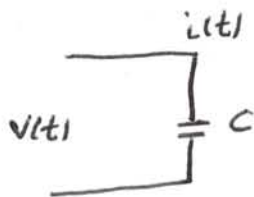

$$i(t) = C \frac{dv(t)}{dt}$$

$\swarrow$
 Farads (F)



3 - Inductor:

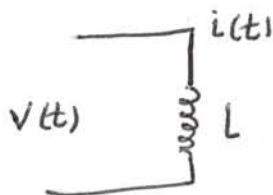

$$v(t) = L \frac{di(t)}{dt}$$

$\swarrow$
 Henry (H)


DC Versus AC:

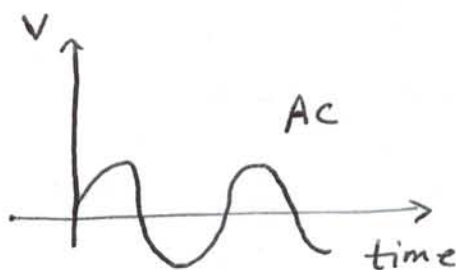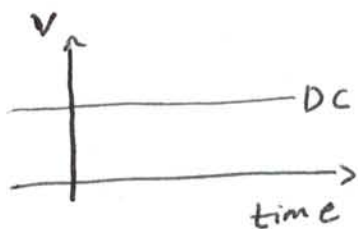

f : frequency
(Hertz or Hz)

ω : angular f
 $= 2\pi f$

Example:

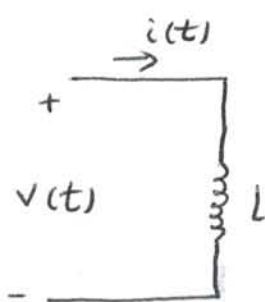

$$v(t) = V \sin(\omega t)$$

$$\Rightarrow i(t) = \text{Vanishing term} + \text{sinusoidal term}$$

- How to get the steady-state term:
- Use Fourier transform

$$v(t) \rightarrow V, \quad i(t) \rightarrow I$$

$$\Rightarrow 1 - \text{Resistor}$$

$$V = IR$$


$$2 - \text{Inductor}$$

$$V = (2\pi f j) L I = (\omega j L) I$$

$$3 - \text{Capacitor}$$

$$I = (2\pi f j) C V = (\omega j C) V$$

Impedance:

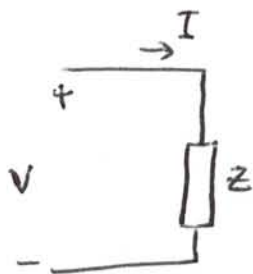

$$Z = R + jX$$





$\swarrow$ resistance $\searrow$ reactance

$$V = Z I$$


$$Z_R = R, \quad Z_L = j\omega L, \quad Z_C = \frac{1}{j\omega C}$$

Kirchhoff's Laws:

$$KCL, KVL$$

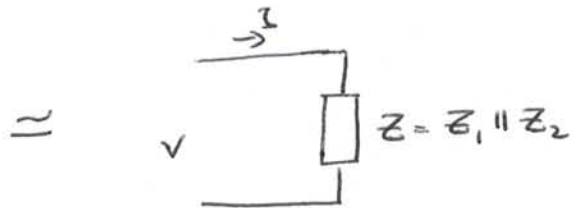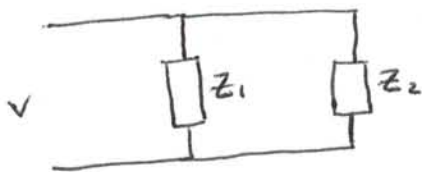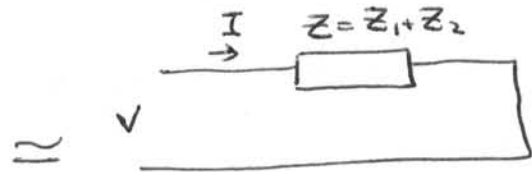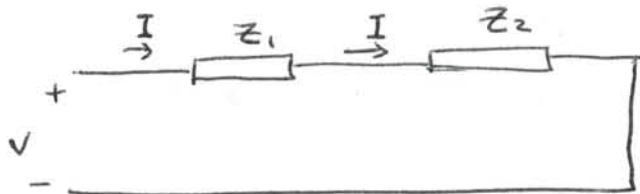

- Instantaneous power:

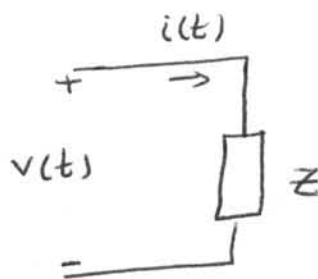

$$p(t) = v(t) i(t)$$

Assume that:

$$v(t) = V_{\max} \cos(\omega t + \theta_v)$$

$$i(t) = I_{\max} \cos(\omega t + \theta_i)$$

$$\Rightarrow p(t) = \frac{1}{2} V_{\max} I_{\max} (\cos(\theta_v - \theta_i) + \cos(2\omega t + \theta_v + \theta_i))$$

Note that:

- First term is constant.

- second term has zero average.

- phasor representation:

$$v(t) = V_{\max} \operatorname{Re}(e^{j\omega t} e^{j\theta_v}) \Rightarrow \underset{\text{phasor}}{V} = \frac{V_{\max} e^{j\theta_v}}{\sqrt{2}}$$

$$\Rightarrow V = |V| \cos \theta_v + j|V| \sin \theta_v$$



- Active power:
$$P = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{2} V_{\max} I_{\max} \cos \varphi$$
$$= \operatorname{Re}(VI^*)$$

- Reactive power:
$$Q = \operatorname{Im}(VI^*)$$


- Complex power: $S = V I^* = P + Qi$

- Apparent power: $|S| = \sqrt{P^2 + Q^2}$

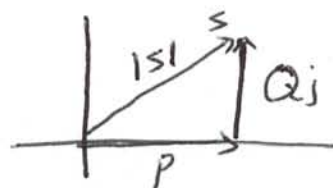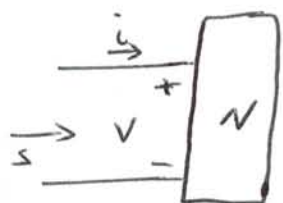- Power Factor: $\cos \varphi = \cos(\angle S)$



why $\sqrt{2}$?

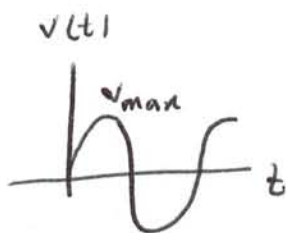

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v(t)^2 dt} = \frac{V_{max}}{\sqrt{2}}$$

Units:

P : Watts (W, kW, MW)

Q : Voltamperes reactive (VAR, kVAR, MVAR)

S : Voltamperes (VA, kVA, MVA)

$|S|$: Volt amperes (VA, kVA, MVA)

Examples:

- resistor: $S = V I^* = (Z I) I^* = |I|^2 R$

$$\Rightarrow P = |I|^2 R, Q = 0$$

- Inductor: $S = (j\omega L I) I^* = j\omega L |I|^2$

$$\Rightarrow P = 0, Q = \omega L |I|^2$$

- Capacitor: $S = \left(\frac{I}{j\omega C}\right) I^* = -\frac{1}{\omega C} j |I|^2$

$$\Rightarrow P = 0, Q = \frac{|I|^2}{\omega C}$$

Note that: - Resistor consumes active power
(converts to heat)

- Inductor consumes reactive power

- Capacitor generates reactive power

Connection between $p(t)$ and P/Q ?

- Inductor: Assume that $i(t) = \sqrt{2} |I| \cos(\omega t + \theta)$

$$\Rightarrow v(t) = L \frac{di(t)}{dt} = -\sqrt{2} \omega L |I| \sin(\omega t + \theta)$$

$$\begin{aligned} \Rightarrow p(t) &= v(t) i(t) = -\omega L |I|^2 \sin(2\omega t + 2\theta) \\ &= -Q \sin 2(\omega t + \theta) \end{aligned}$$

Reactive power: goes back and forth in the network

Max magnitude: Q

- General case : $i(t) = \sqrt{2} |I| \cos \omega t$



$$\Rightarrow p(t) = v(t) i(t) = [\sqrt{2} |I| |Z| \cos(\omega t + \phi_Z)] i(t)$$

$$= |Z| |I|^2 (\cos(\phi_Z) + \cos(2\omega t + \phi_Z))$$

$$= |Z| |I|^2 (\cos(\phi_Z) + \cos(2\omega t) \cos \phi_Z - \sin(2\omega t) \sin \phi_Z)$$

$$= P(1 + \cos 2\omega t) - Q \sin 2\omega t$$

$$= \text{Term 1} + \text{Term 2}$$

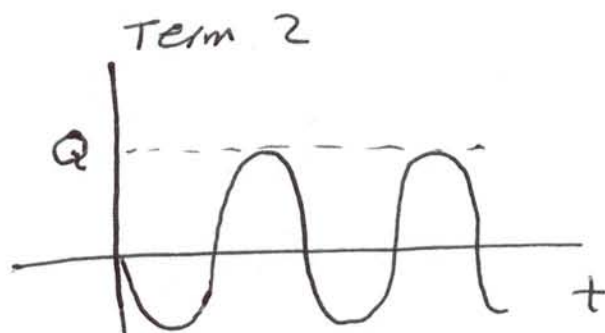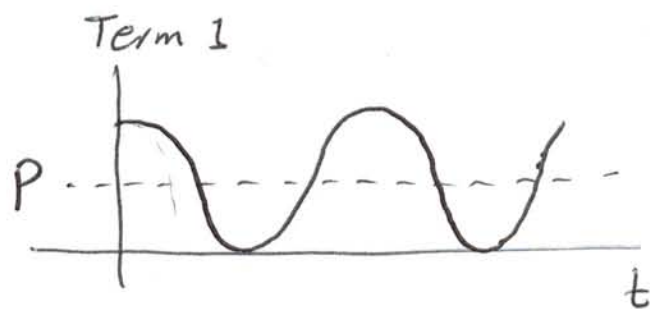

- Two ways to get S :


$$1. \quad S = V I^* = (Z I) I^* = |I|^2 Z$$

$$\Rightarrow P = R |I|^2, \quad Q = X |I|^2$$

$$2. \quad S = V I^* = (V) \left(\frac{V}{Z} \right)^* = \frac{|V|^2}{Z^*}$$

$$\Rightarrow P = G |V|^2, \quad Q = B |V|^2$$

- Example:

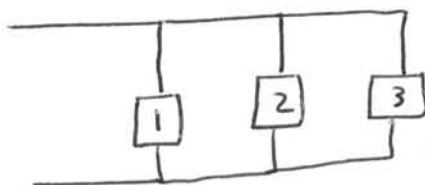

8

- Three loads are connected across a 480 V (rms) Line
- Load 1 absorbs 12 kW and 6.667 KVAR.
- Load 2 absorbs 4 KVA at 0.96 PF leading. $\rightarrow (\underline{I} \text{ leads } \underline{V})$
- Load 3 absorbs 15 kW at unity power factor.
- Find equivalent impedance?


$$S_1 = 12 + j6.667 \text{ KVA}$$

$$S_2 = 4(0.96 - j\sin(\cos^{-1}0.96)) \text{ KVA}$$


$$S_3 = 15(1 + j0) \text{ KVA}$$

$$S_i = \frac{|\underline{V}|^2}{\underline{Z}_i^*} \Rightarrow \text{Find } \underline{Z}_i \Rightarrow \frac{1}{\underline{Z}} = \sum \frac{1}{\underline{Z}_i}$$

Conservation of Energy:

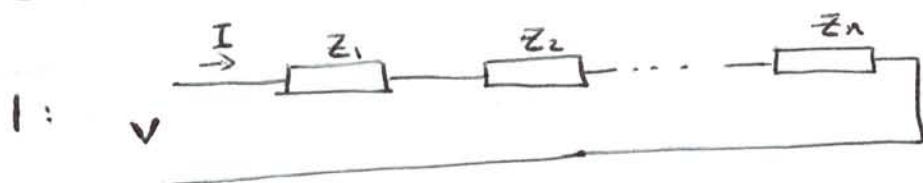


$$\begin{aligned} S_i &= \underline{Z}_i |\underline{I}|^2 \Rightarrow \sum S_i = (\sum \underline{Z}_i) |\underline{I}|^2 \\ &= (\sum \underline{Z}_i) \underline{I} \underline{I}^* \\ &= \underline{V} \underline{I}^* = S \end{aligned}$$

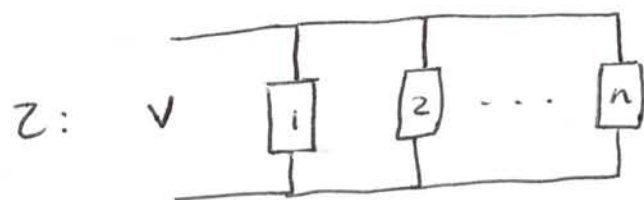

$$S_i = V I_i^* = \frac{|V|^2}{Z_i^*}$$

$$S = V I^* = V (\sum I_i)^* = \sum V I_i^* = \sum S_i$$


3: General case

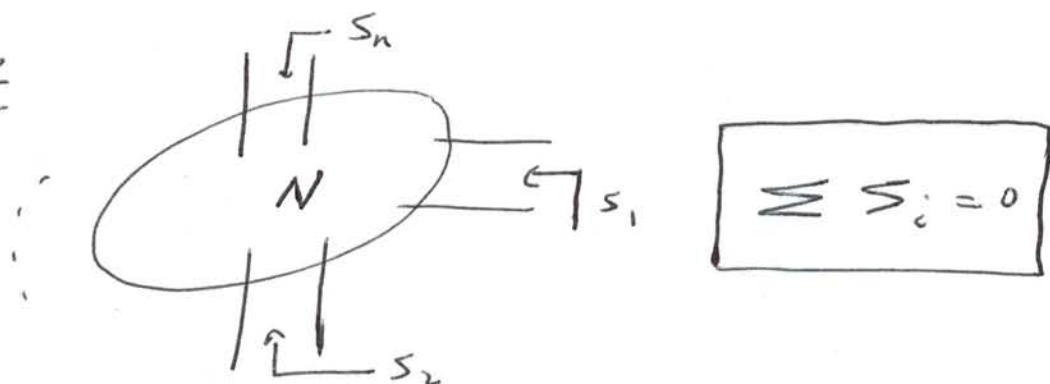

N : passive network (say $R, L, C, \dots$)

(Active network generates active power)

Example:

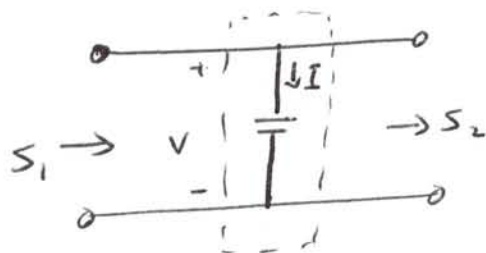

$$S_2 - S_1 = -j\omega C |V|^2$$

$$\Rightarrow P_2 = P_1, \quad Q_2 = Q_1 + \omega C |V|^2$$

- Capacitor (bank) at a bus injects reactive power into the network.

Example:



$$S_2 - S_1 = j\omega L |I|^2$$

- Short transmission line consumes reactive power.