

- what happens if $|V_1| = |V_2|$ (thru control (10) from outside world)


$$P_1 = P_2, \quad Q_2 = Q_1 - \omega L |I|^2$$

$$S_1 = V_1 I^*, \quad S_2 = V_2 I^* \quad \xRightarrow{|V_1| = |V_2|} \quad |S_1| = |S_2|$$

$$\Rightarrow P_1^2 + Q_1^2 = P_2^2 + Q_2^2 \quad \Rightarrow Q_2 = -Q_1$$


$$\Rightarrow \boxed{S_2 = S_1^*}$$

Symbols:


- Generator: 

- BUS 

- Load (constant power) 

- Transmission Line 

Example:

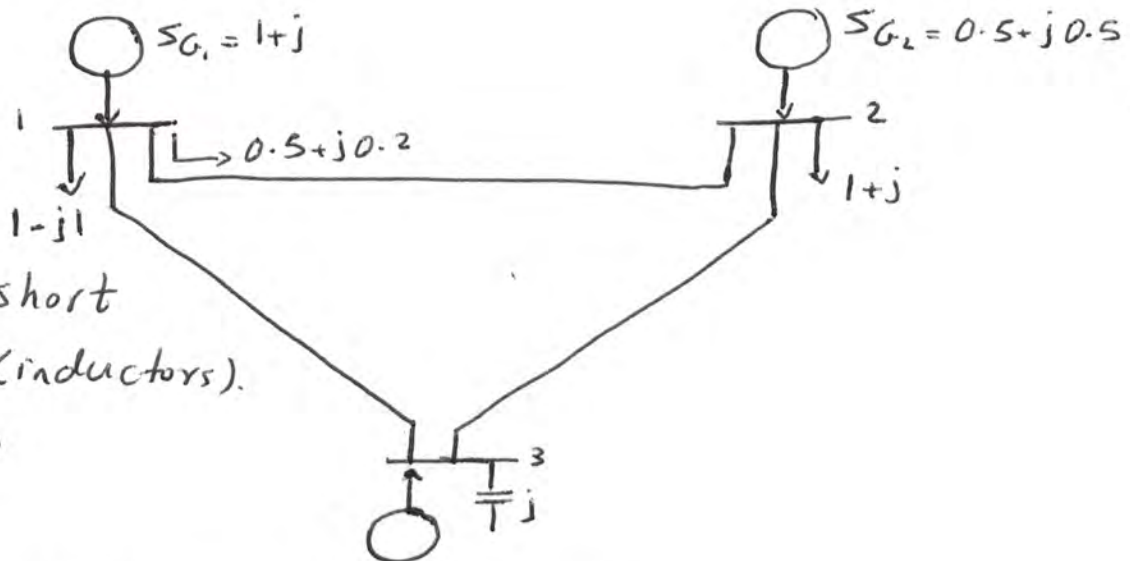

- Lines are short (inductors).

- Find S_{G_3} ?

$$S_{13} = S_{G_1} - (1-j) - (0.5 + j0.2) = -0.5 + j1.8$$


$$S_{31} = -S_{13}^* = 0.5 + j1.8$$

$$S_{23} = S_{G2} - (1+j) - (-S_{12}^*) = -j0.7$$

$$S_{32} = -S_{23}^* = -j0.7$$


$$\Rightarrow S_{G3} = S_{32} + S_{12} = \underline{\underline{0.5 + j0.1}}$$

- Power Transfer:

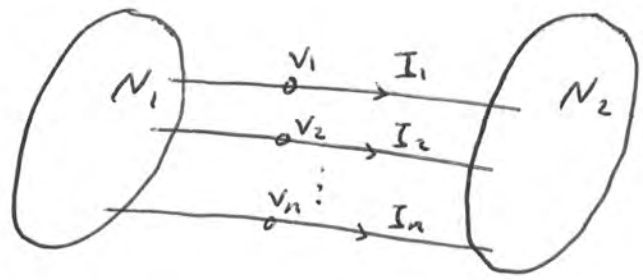

power transferred from N_1 to N_2
 $= S = \sum V_i I_i^*$

Balanced Three-phase Network:

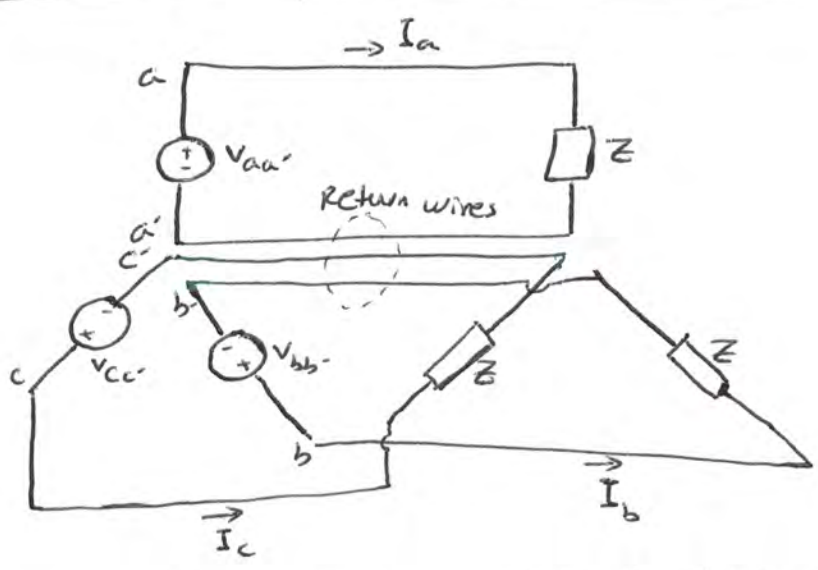

- connect a, b, c
- connect a', b', c'

Balanced $\exists \phi$: $- |V_{aa'}| = |V_{bb'}| = |V_{cc'}|$

- Angle difference is ± 120 (for every two phases)


Then : $I_a + I_b + I_c = 0 \Rightarrow$ No current on return wire

Remove the return wires:

- Saving in wiring
- less loss ($W_{ss} = |I|^2 r$)

Balanced 3 ϕ = balanced sources + balanced loads (Z)

Example:

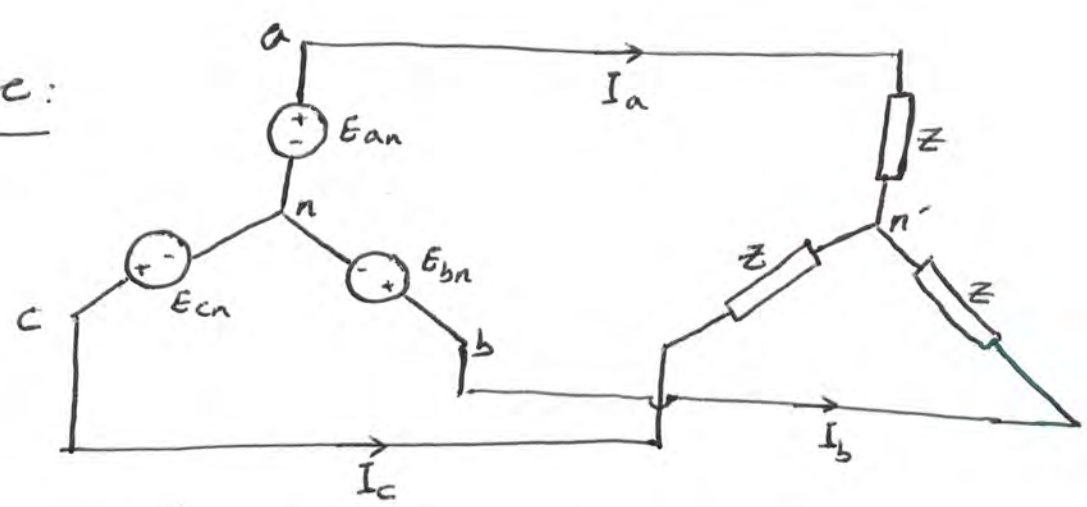

Calculate $V_{nn'}$?
(neutral-neutral voltage)

$$I_a = \frac{E_{an} + V_{nn'}}{Z}$$

$$I_b = \frac{E_{bn} + V_{nn'}}{Z}, \quad I_c = \frac{E_{cn} + V_{nn'}}{Z}$$



$$I_a + I_b + I_c = 0, \quad E_{an} + E_{bn} + E_{cn} = 0 \quad (\text{why?})$$

$$\Rightarrow \frac{3V_{nn'}}{Z} = 0 \Rightarrow V_{nn'} = 0$$

- what if n is connected to n' via an impedance Z_n ?


$$I_{nn'} = \frac{V_{nn'}}{Z_n} \Rightarrow \left(\frac{3}{Z} + \frac{1}{Z_n} \right) V_{nn'} = 0$$
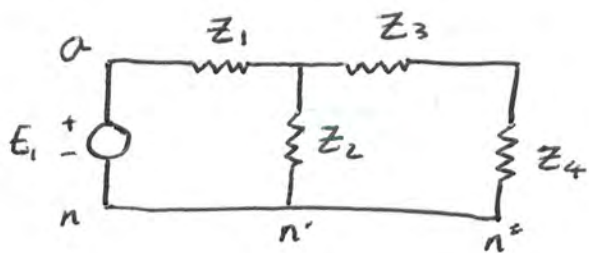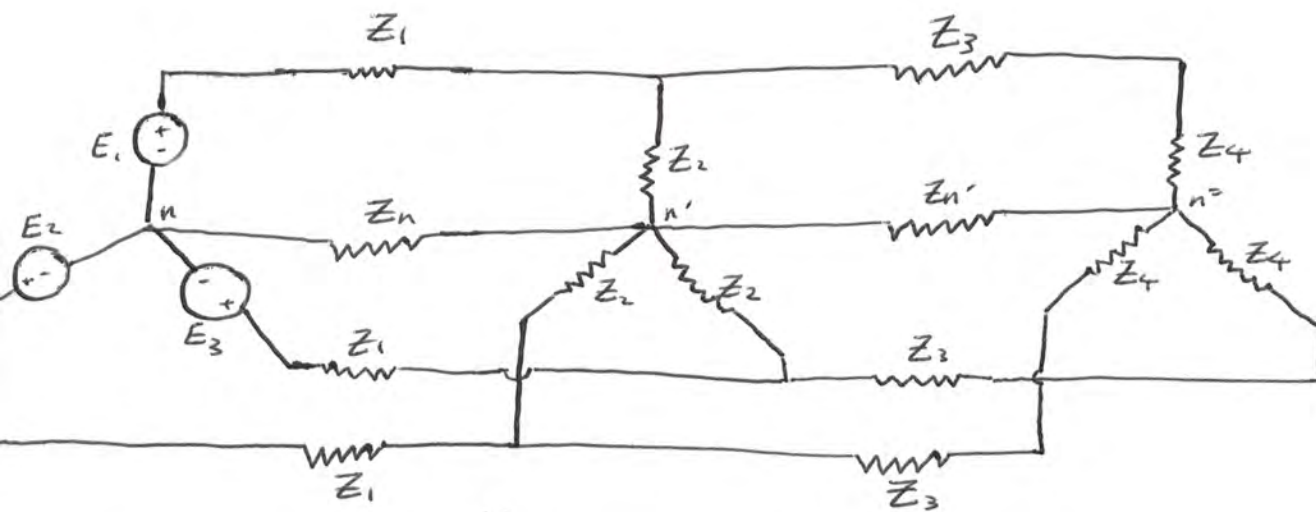
$$\Rightarrow \text{If } \frac{3}{Z} + \frac{1}{Z_n} = 0, \text{ then } V_{nn'} = 0$$




per phase analysis

Delta-Wye Load Transformation:

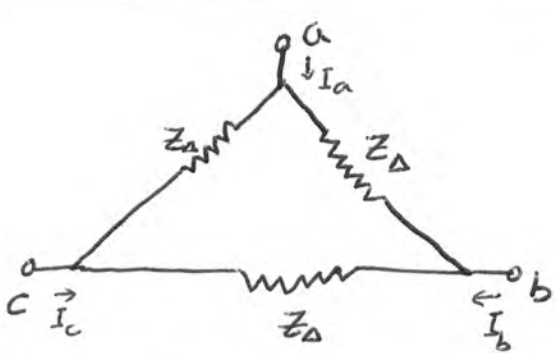

Δ-Y Trans.
↔

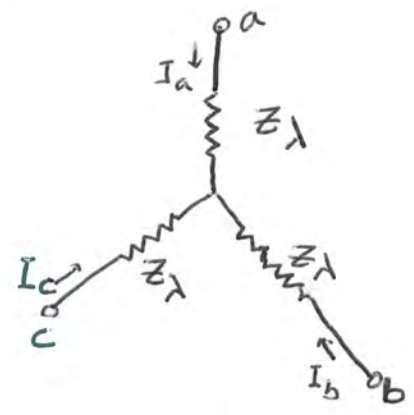

$$I_a = \frac{V_{ab}}{Z_{\Delta}} + \frac{V_{ac}}{Z_{\Delta}} = \frac{V_{ab} + V_{ac}}{Z_{\Delta}}$$

$$V_{ab} = Z_{\lambda} (I_a - I_b)$$



$$V_{ac} = Z_{\lambda} (I_a - I_c)$$

$$\Rightarrow V_{ab} + V_{ac} = Z_{\lambda} (I_a + 2I_a)$$



$$Z_{\Delta} = 3Z_{\lambda}$$

Delta-Wye source Transformation:

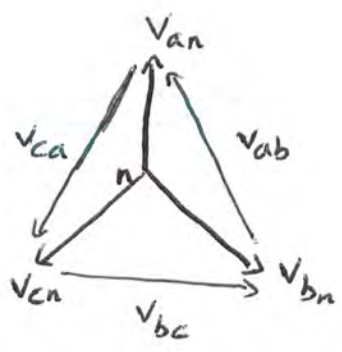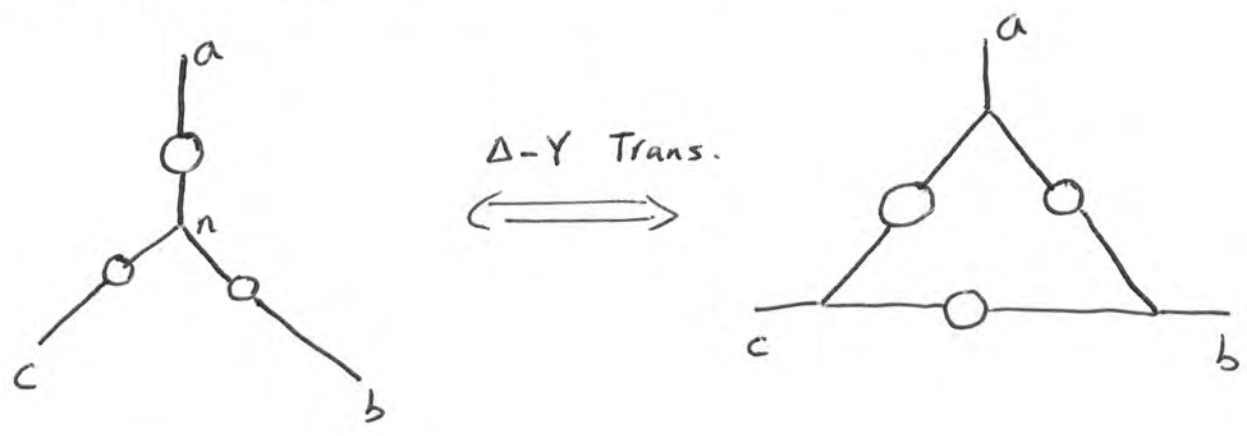


$$\Rightarrow V_{ab} = \sqrt{3} V_{an} e^{j\pi/6}$$

V_{ab} = Line-Line voltage
= line voltage


V_{an} = Line-Neutral voltage
= phase voltage

$$\Rightarrow |\text{Line voltage}| = \sqrt{3} |\text{phase voltage}|$$

Example:

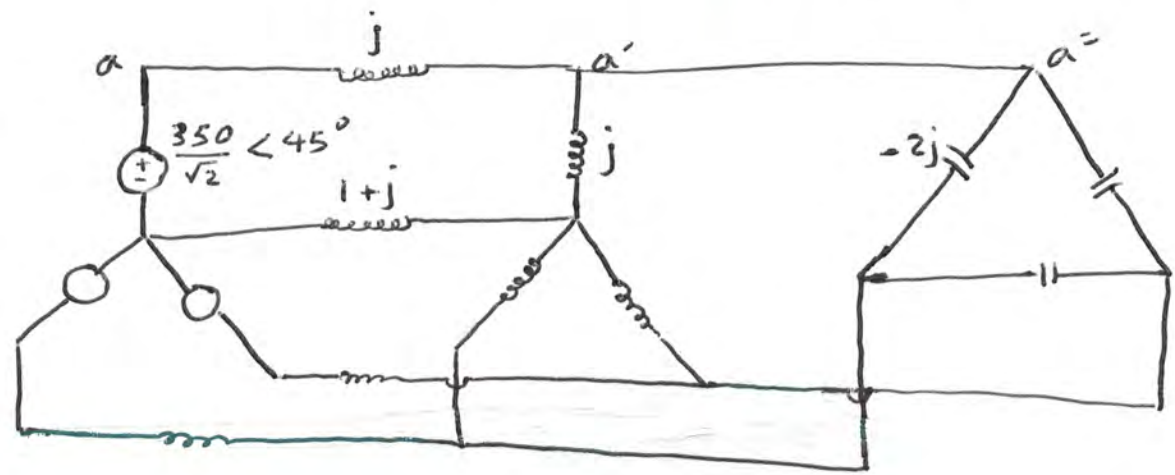

per phase

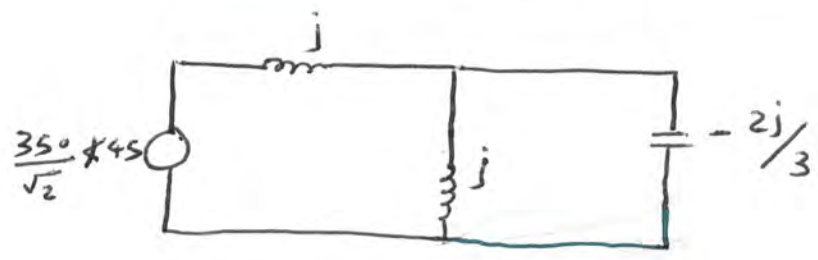

3 ϕ power:

(15)


$$\begin{aligned} S_{3\phi} &= V_a I_a^* + V_b I_b^* + V_c I_c^* \\ &= V_a I_a^* + V_a e^{-j\frac{2\pi}{3}} I_a^* e^{j\frac{2\pi}{3}} + V_a e^{j\frac{2\pi}{3}} I_a^* e^{-j\frac{2\pi}{3}} \\ &= 3 V_a I_a^* = 3 S \end{aligned}$$

$$\begin{aligned} P_{3\phi}(t) &= V_a(t) i_a(t) + V_b(t) i_b(t) + V_c(t) i_c(t) \\ &= |V||I| \left(\cos\phi + \cos(2\omega t + \phi_V + \phi_I) \right. \\ &\quad \left. + \cos\phi + \cos(2\omega t + \phi_V + \phi_I - \frac{4\pi}{3}) \right. \\ &\quad \left. + \cos\phi + \cos(2\omega t + \phi_V + \phi_I + \frac{4\pi}{3}) \right) \\ &= 3|V||I| \cos\phi = 3P = \underline{\underline{\text{Constant}}} \end{aligned}$$

\Rightarrow Instantaneous power delivered to load is constant.


Application in ac motor: constant speed

Question: what to do with this?

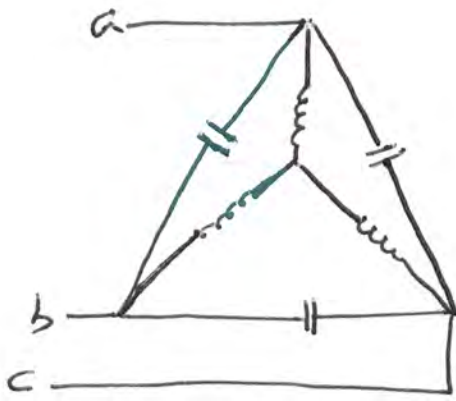

Transmission Lines:

Distributed mode L:

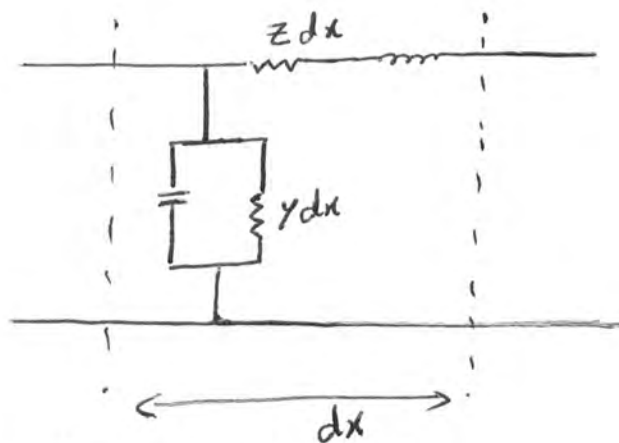

$Z = r + j\omega l =$ series impedance per meter

$Y = g + j\omega c =$ shunt admittance per meter (to neutral)


$\gamma = \sqrt{YZ} =$ propagation constant

$Z_c = \sqrt{Z/Y} =$ characteristic impedance

$m =$ length (meter)



lumped model

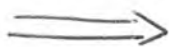

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} \cosh \gamma m & Z_c \sinh \gamma m \\ \frac{\sinh \gamma m}{Z_c} & \cosh \gamma m \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

Example: - A 60 Hz 138 kV 3 ϕ line is 225 mi long

- distributed line parameters are:

$r = 0.169 \text{ } \Omega/\text{mi}$, $L = 2.093 \text{ mH}/\text{mi}$, $C = 0.014 \text{ } \mu\text{F}/\text{mi}$, $\gamma =$

- It delivers 40 MW at 132 kV with 0.95 power fac lagging

- Find efficiency.

$$\omega = 2\pi f = 2\pi \cdot 60$$

$$Z = 0.169 + j\underline{0.789} \quad , \quad Y = j5.38 \times 10^{-6}$$

$$Z_c = \sqrt{Z/Y} \quad , \quad m\delta = m\sqrt{ZY}$$

$$|V_2| = 132 \times 10^3 / \left(\frac{\sqrt{3}}{\sqrt{3}}\right) = 76.2 \text{ KV}$$


per phase $P_{load} = \frac{40}{3} = 0.95 |V_2| |I_2| \quad , \quad \angle I_2 = -\cos^{-1} 0.95$

Given V_2, I_2 , we can find V_1, I_1 .

$$P_{12} = \text{Re } V_1 I_1^* = 14.45 \text{ MW}$$

$$\Rightarrow \eta = \frac{13.33}{14.45} = 0.92 \Rightarrow \text{Efficiency} = 92\%$$

- lumped circuit Equivalent: (π model)

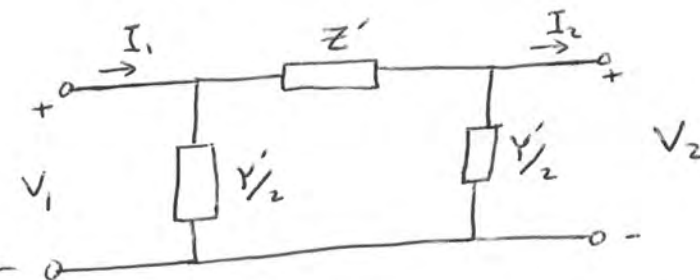


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$

$$V_1 = V_2 + Z' \left(I_2 + \frac{V_2 Y'}{2} \right) = \underbrace{\left(1 + \frac{Z' Y'}{2} \right)}_A V_2 + \underbrace{Z'}_B I_2$$

$$I_1 = \frac{Y' V_1}{2} + I_2 + V_2 \frac{Y'}{2} = \underbrace{Y' \left(1 + \frac{Z' Y'}{4} \right)}_C V_2 + \underbrace{\left(1 + \frac{Z' Y'}{2} \right)}_D I_2$$

- π -equivalent model is commonly used.


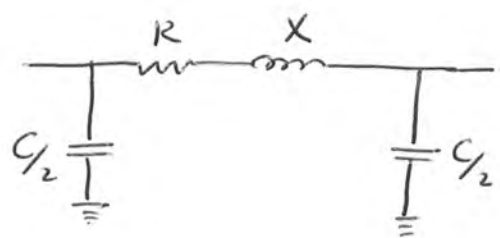
- long line ($m > 150$ mi): Use exact π model
- medium line ($50 < m < 150$):




C : total capacitance
 R : total resistance
 X : total inductance

- short line ($m < 50$): Remove C .

Example:

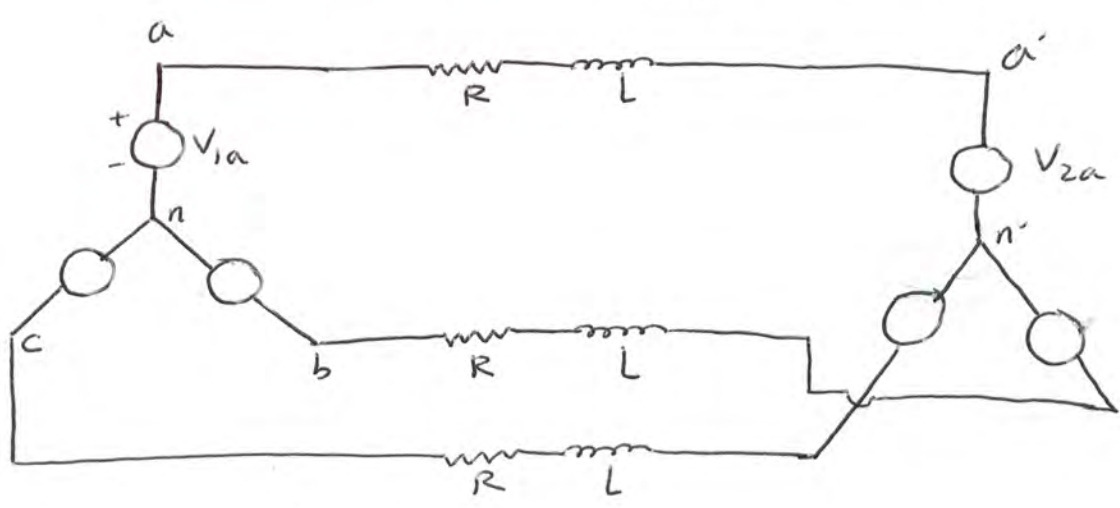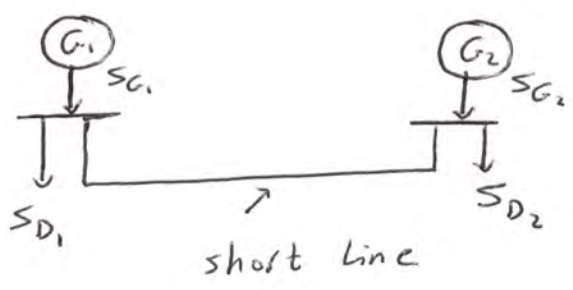
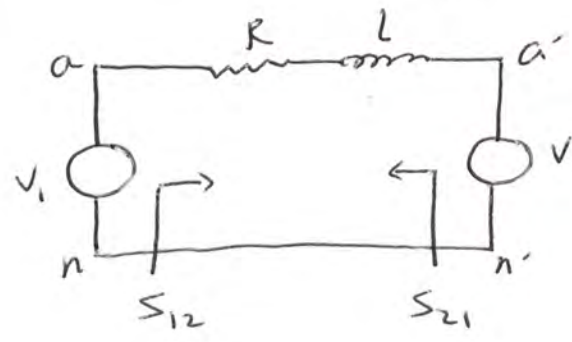
$$\theta_{12} = \theta_1 - \theta_2 (\angle V_1 - \angle V_2)$$



$$\Rightarrow S_{12} = V_1 I_1^* = V_1 \left(\frac{V_1 - V_2}{Z} \right)^*$$


$$= \frac{|V_1|^2}{|Z|} e^{j\phi Z} - \frac{|V_1||V_2|}{|Z|} e^{j(\phi Z + \theta_1)}$$

and

$$S_{21} = \frac{|V_2|^2}{|Z|} e^{j\phi Z} - \frac{|V_2||V_1|}{|Z|} e^{j(\phi Z - \theta_1)}$$

- what's $S_{12} + S_{21}$? Transmission loss

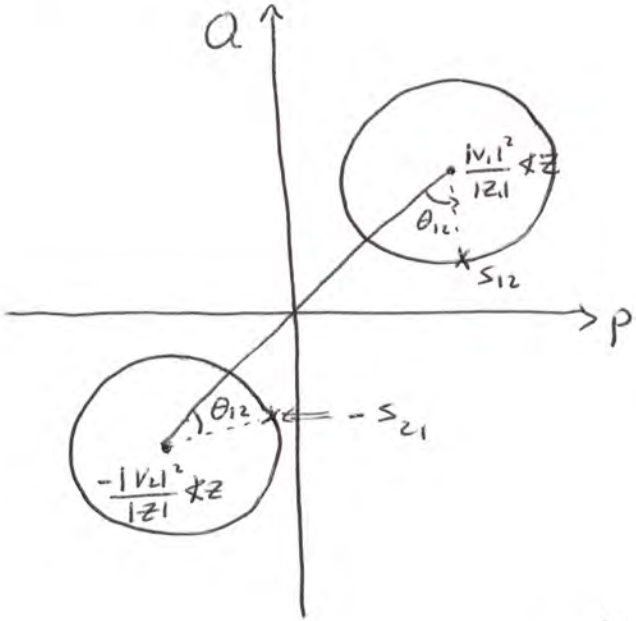- In the p-Q plane, draw S_{12} and $-S_{21}$:



- If $|V_1| \neq |V_2|$, then the circles do not intersect:

$$\frac{|V_1|^2 + |V_2|^2}{|Z|} > \frac{|V_1||V_2|}{|Z|} \times 2$$

- As θ_{12} increases from zero, active power sent/received increases.

- Max active power received happens at $\theta_{12} = \angle Z$
- max active power sent happens at $\theta_{12} = 180^\circ - \angle Z$

- $R=0$ and $Z=jX$:

$$P_{12} = -P_{21} = \frac{|V_1||V_2|}{X} \sin \theta_{12}$$

$$Q_{12} = \frac{|V_1|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12}$$

$$Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12}$$

\Rightarrow ultimate transmission capacity = $\frac{|V_1||V_2|}{X}$

- ways to increase capacity:
- 1- Increase voltage level
 - 2- Decrease X (series compensation)