

- Normal operating condition for high voltage line: (20)

$$|V_1| \approx |V_2|, \quad \angle Z \approx 90^\circ, \quad \theta_{12} = \text{small} (< 10^\circ)$$

$\Rightarrow$ Decoupling between control of active and reactive powers:

- P_{12} : couples strongly with θ_{12}
- Q_{12} : couples strongly with $|V_1| - |V_2|$

$$\Delta P_{12} \Big|_{1,1,0} = \frac{|V_1||V_2|}{X} \Delta \theta_{12}$$

$$\Delta Q_{12} \Big|_{1,1,0} = \frac{|V_1|}{X} (\Delta |V_1| - \Delta |V_2|)$$

Example: - Balanced 3 ϕ transmission line with $Z = 1 \angle 85^\circ$, $\theta_{12} = 10^\circ$

- Find S_{12} and $-S_{21}$ for


$$1 - |V_1| = |V_2| = 1$$

$$2 - |V_1| = 1.1, |V_2| = 0.9$$

$$1 - S_{12} = 0.1743, \quad -S_{21} = 0.1717 - j0.0303$$

$$2 - S_{12} = 0.1917 + j0.2192, \quad -S_{12} = 0.1856 + j0.1493$$

Example:

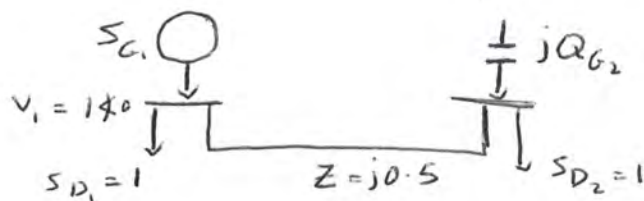

1 - pick Q_{G2} so that $|V_2| = 1$.

2 - what happens if $Q_{G2} = 0$?

$$1) P_{12} = -P_{21} = 1$$

$$P_{12} = \frac{|V_1||V_2|}{X} \sin \theta_{12} \Rightarrow \theta_{12} = 30^\circ$$

$$Q_{G2} = Q_{21} = \frac{|V_2|^2}{X} - \frac{|V_1||V_2|}{X} \cos \theta_{12} = 0.268$$


$$Q_{G2} > 0 \Rightarrow C \text{ can be found.}$$

$$2) Q_{G2} = 0 \Rightarrow S_{21} = -1$$



$$\Rightarrow (2|V_2|^2)^2 + 1^2 = (2|V_2|)^2$$

$$\Rightarrow V_2 = 0.707 \angle -45^\circ$$

This is voltage drop.

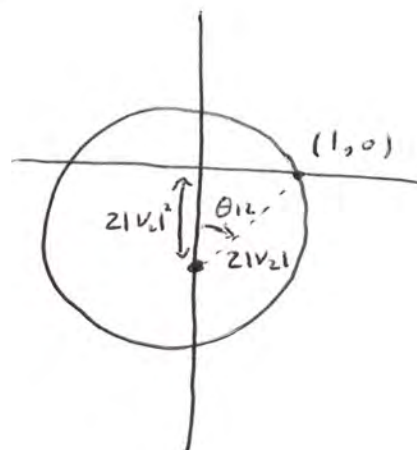

Voltage collapse:

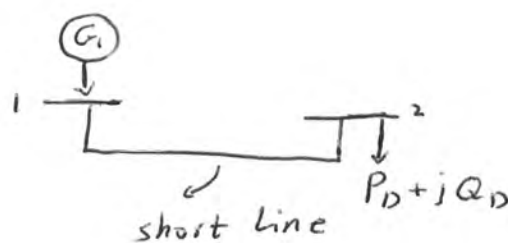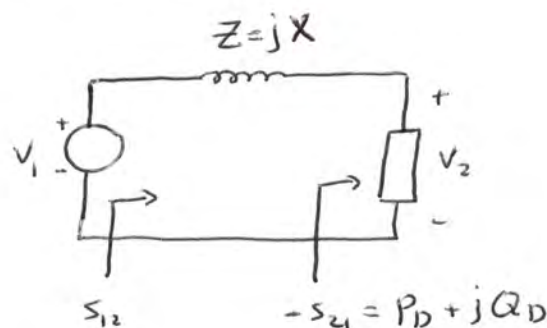

$$P_D = P_{12} = \frac{|V_1||V_2|}{X} \sin \theta_{12}$$

$$Q_D = -Q_{21} = -\frac{|V_2|^2}{X} + \frac{|V_2||V_1|}{X} \cos \theta_{12}$$


Eliminate θ_{12} : $S_D = |V_2||I_2| e^{j\phi} = P_D(1 + j\beta)$

where $\beta = \tan \phi$, $\phi = \angle S_D = \angle V_2 - \angle I_2$

, $\cos \phi = \text{power factor}$


$$\left(\beta P_D + \frac{|V_2|^2}{X} \right)^2 = \left(\frac{|V_2||V_1|}{X} \right)^2 - P_D^2$$

- Assume $|V_1| = 1$ (per unit)

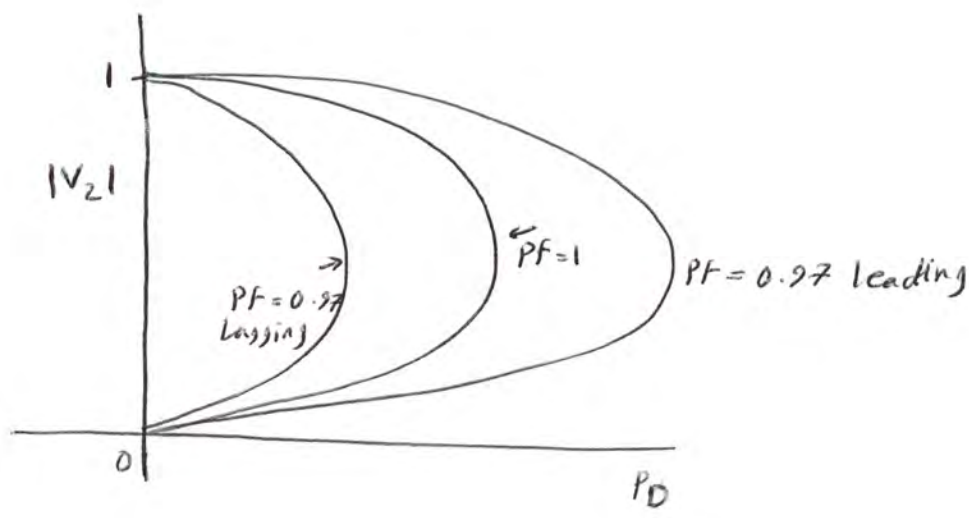

- Look at $|V_2|$ v.s. P_D : There is a point at which "voltage collapse" occurs.

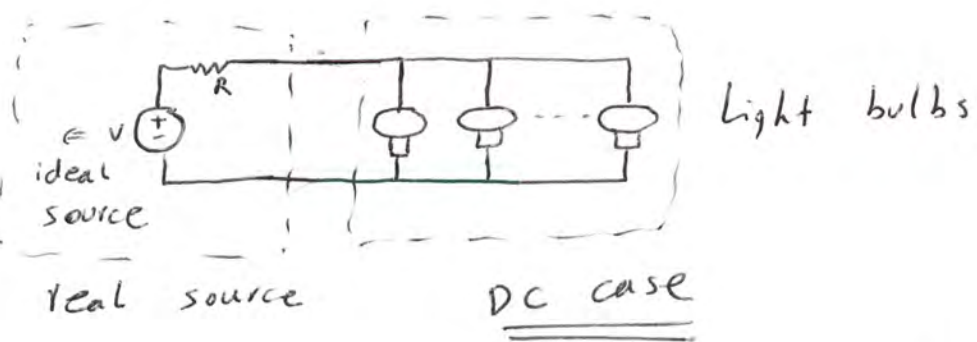- Interpretation: we want to increase a room brightness.




Claim: Adding bulbs increases the brightness up to some point, then the room gets darker!

proof: model light bulb as

$$P_D = \frac{V_D^2}{r} \times n, \quad r_e = \frac{r}{n} \Rightarrow V_D = \frac{r_e}{R + r_e} V = \frac{r}{Rn + r} V$$


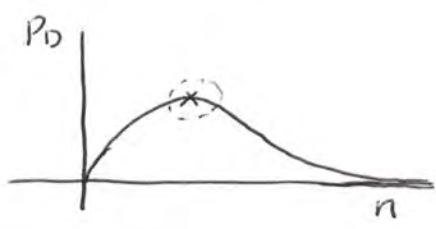
$$\Rightarrow P_D = \frac{V^2 r n}{(Rn + r)^2} \Rightarrow$$




- Generation is typically at line voltages 11-30 kV (23)
- Transmission over long distances requires high voltages, say 138, 230, 345, 765 kV.
- Distribution takes place at low voltages, say 2400 or 41600 V.
- Industrial load needs 440 V.
- Commercial or residential use needs 240/120 V.


Advantages of going to high voltage:

- $P_{12} = \frac{|V_1||V_2|}{X} \sin \theta_{12} \Rightarrow$ transmission capacity increase
- Loss reduction:

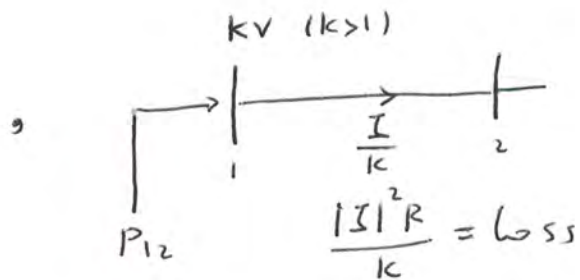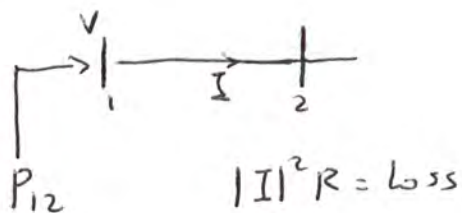

Transformer:

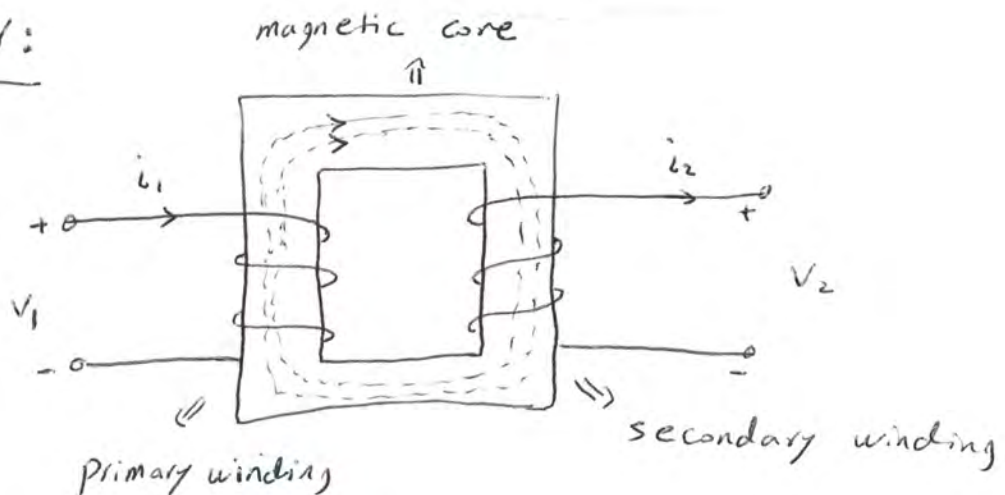


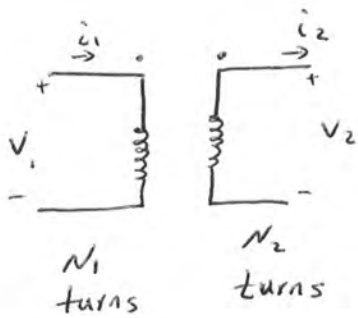


Ideal Trans :

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n, \quad \frac{i_2}{i_1} = \frac{1}{n} = a$$

$$\Rightarrow i_1 V_1 = i_2 V_2 \text{ (lossless device)}$$

Equivalence:

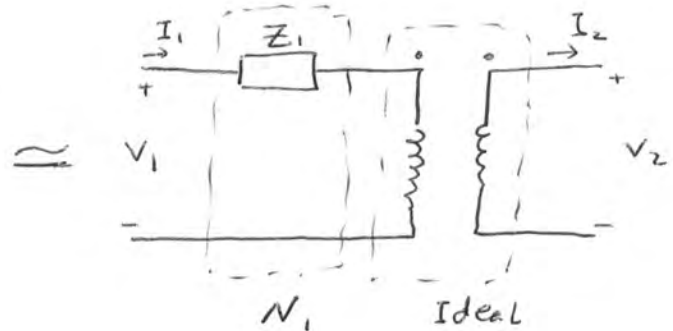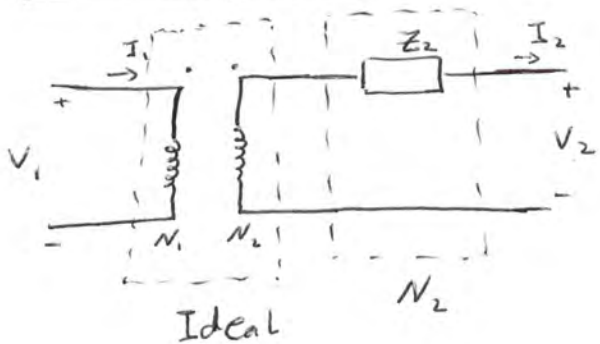


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a & 0 \\ 0 & \frac{1}{a} \end{bmatrix} \begin{bmatrix} 1 & Z_2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}, \quad \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} a & 0 \\ 0 & \frac{1}{a} \end{bmatrix}$$

$$\Rightarrow Z_1 = a^2 Z_2$$

- True even for moving a shunt (not series) impedance

More realistic model:

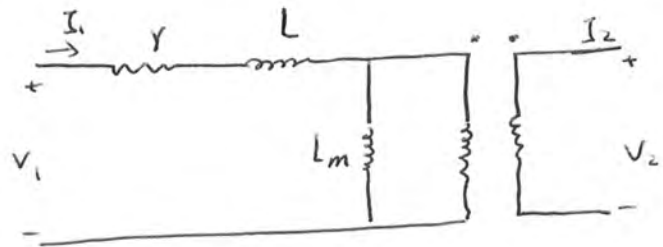


Most of the times, L_m is ignored.


- Various ways to have 3- ϕ transformers.

- Y-Y connection:

(25)

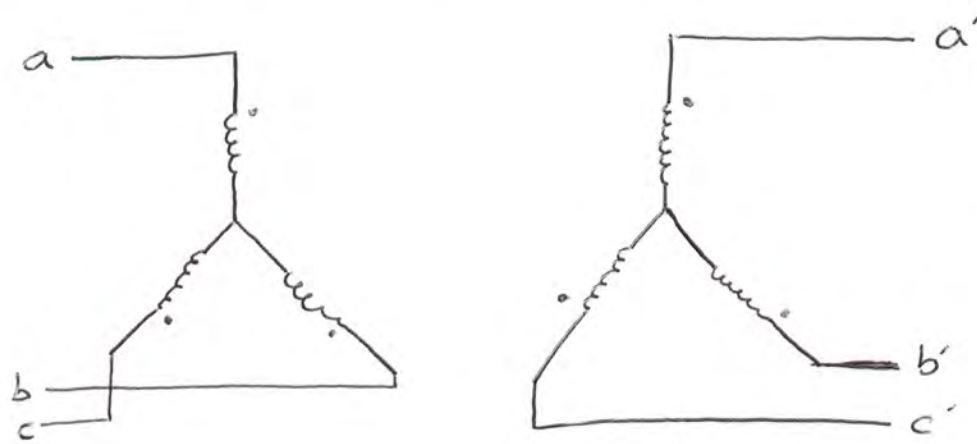


Δ - Δ connection:

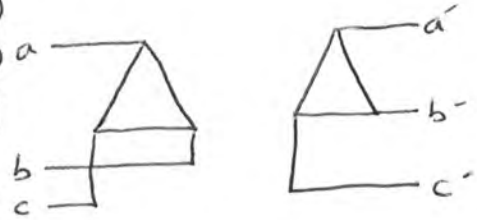

- The above settings just change voltage levels.

- How to change phases?

- Consider Δ -Y connection:

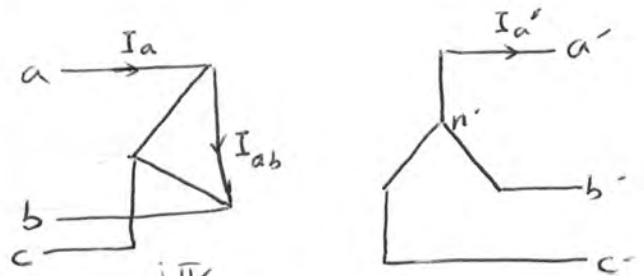

$$V_{a'n'} = n V_{ab} = n (V_{an} - V_{bn}) = \sqrt{3} n e^{j\pi/6} V_{an}$$



$$\Rightarrow \text{gain } k_1 = \sqrt{3} n e^{j\pi/6} \text{ (for every phase)}$$

$$I_a = I_{ab} - I_{ca} = n (I_{a'} - I_{c'}) = \sqrt{3} n e^{-j\pi/6} I_{a'} = k_1^* I_{a'}$$

$$\Rightarrow S' = V_{a'n'} (I_{a'})^* = k_1 V_{an} \left(\frac{I_a}{k_1^*} \right)^* = V_{an} I_a^* = S$$


one-line diagram:

- per phase Analysis:

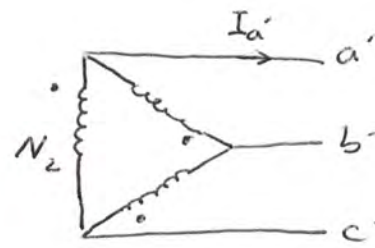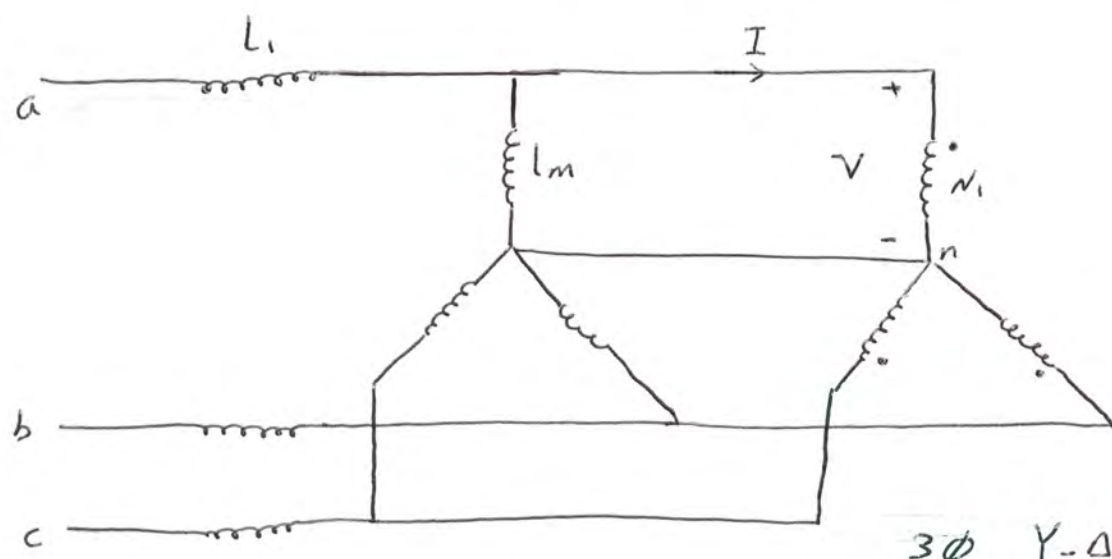

3φ Y-Δ connection


⇓ per phase circuit

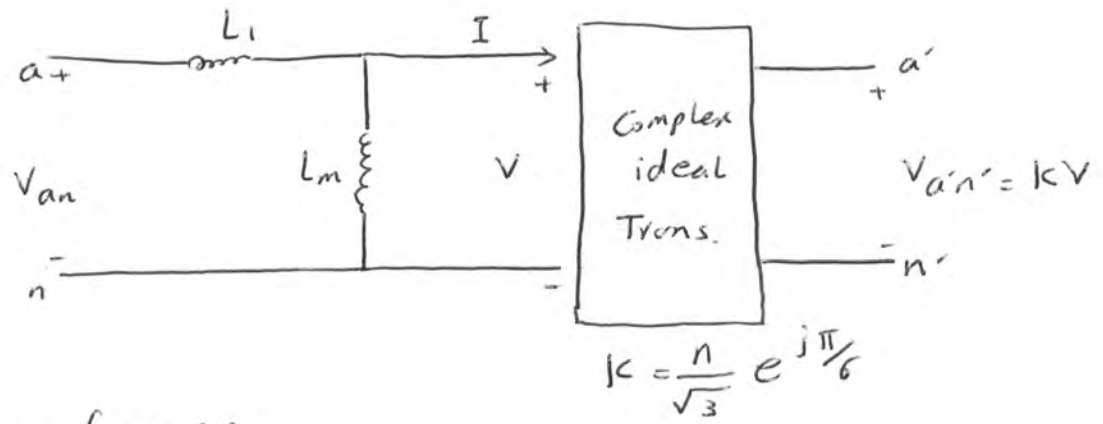

- Auto-transformer:




- Tap-changing Transformer:

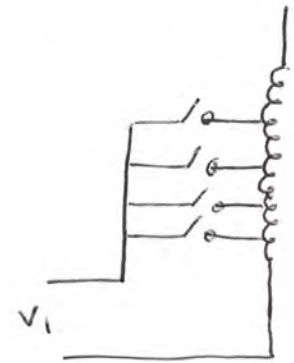

- How to change phases?


- phase-shifting Transformer:

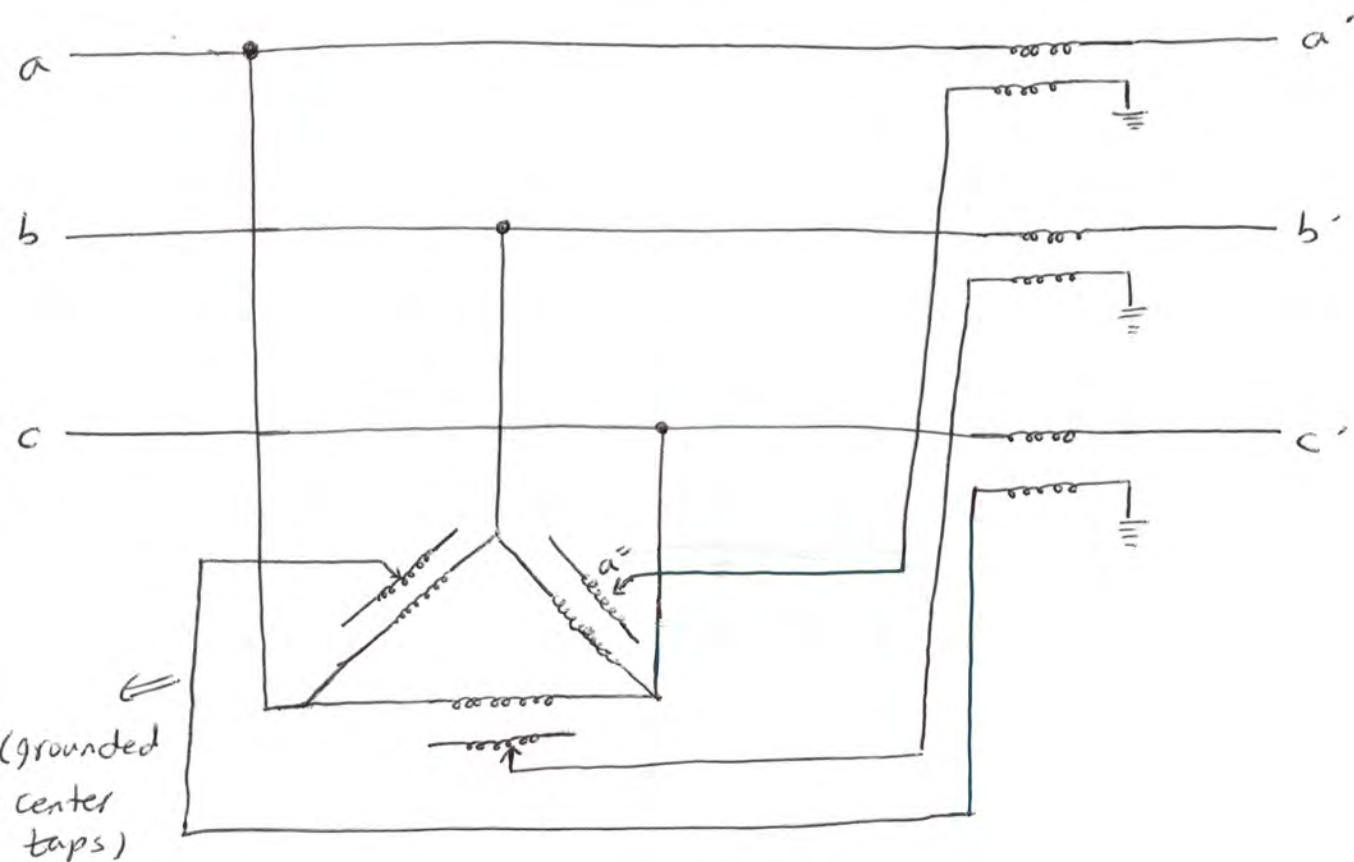(phase shifter: Transformer with unity gain)




$$V_a - V_{a'} = n_2 V_{a''} = n_2 n_1 (V_b - V_c)$$

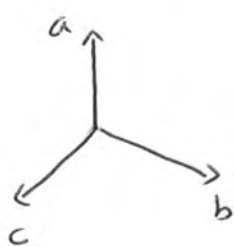
$$\Rightarrow V_{a'} = V_a - n (V_b - V_c)$$




$\Rightarrow$

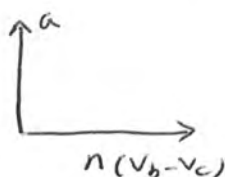


$\Rightarrow$

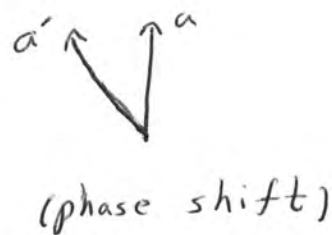

- Application: (Routing power)

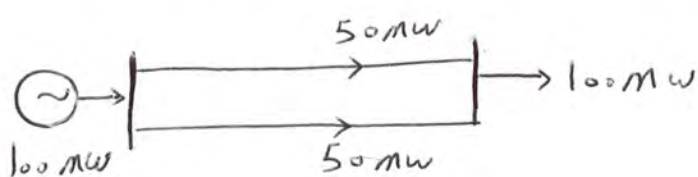


$\Rightarrow$

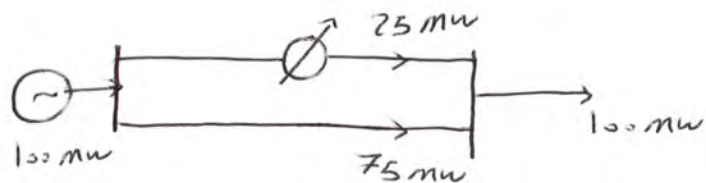



Transformer + Transmission Lines:

(28)

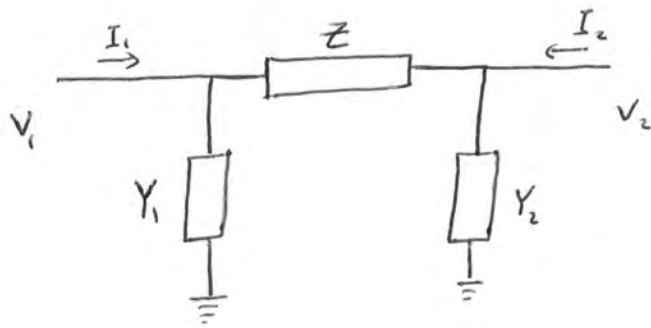

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_1 + \frac{1}{Z} & -\frac{1}{Z} \\ -\frac{1}{Z} & Y_2 + \frac{1}{Z} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

Consider:

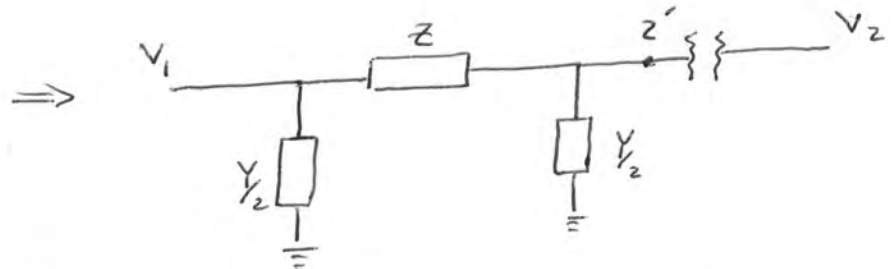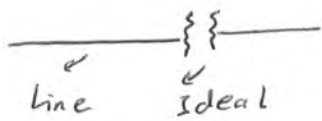


$$\begin{bmatrix} I_1 \\ I_2' \end{bmatrix} = \begin{bmatrix} \frac{Y}{2} + \frac{1}{Z} & -\frac{1}{Z} \\ -\frac{1}{Z} & \frac{Y}{2} + \frac{1}{Z} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2' \end{bmatrix}, \quad V_2' = a V_2, \quad I_2' = \frac{1}{a^*} I_2$$

$$\Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{Y}{2} + \frac{1}{Z} & -\frac{a}{Z} \\ -\frac{a^*}{Z} & (\frac{Y}{2} + \frac{1}{Z}) a a^* \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$B = \frac{Y}{j}$ is called
Line charging.

Assume $a = a^*$ (no phase shifter):

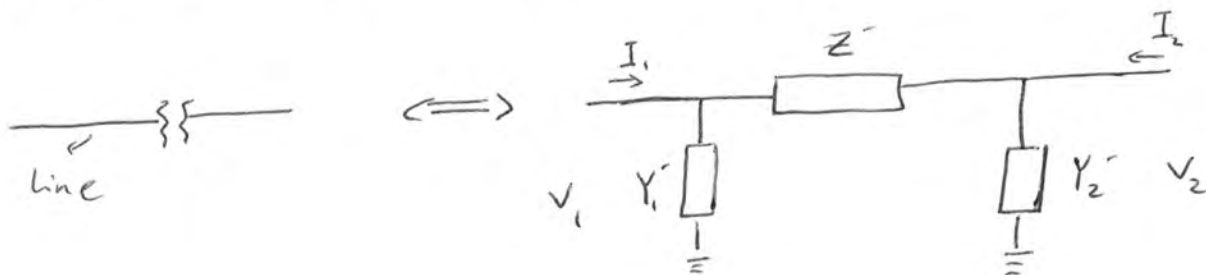

$$Z' = \frac{Z}{a}, \quad Y_1' = \frac{Y}{2} + \frac{1-a}{Z}, \quad Y_2' = \frac{a^2 Y}{2} + \frac{a(a-1)}{Z}$$

- If $a \neq 1$, we are adding a negative shunt resistance